

```
// D Flip-Flop module
module D_FF (
    input wire clk,
    input wire reset,
    input wire D,
    output reg Q,
    output reg Q_bar
);

    always @(posedge clk or posedge reset) begin
        if (reset) begin
            Q <= 1'b0;
            Q_bar <= 1'b1;
        end else begin
            Q <= D;
            Q_bar <= ~D;
        end
    end

endmodule
```

```
// T Flip-Flop module
module T_FF (
    input wire clk,
    input wire reset,
    input wire T,
    output reg Q,
    output reg Q_bar
);

    always @(posedge clk or posedge reset) begin
        if (reset) begin
            Q <= 1'b0;
            Q_bar <= 1'b1;
        end else begin
            case (T)
                1'b0: begin
                    Q <= Q;
                    Q_bar <= Q_bar;
                end
                1'b1: begin
                    Q <= ~Q;
                    Q_bar <= ~Q_bar;
                end
            endcase
        end
    end

endmodule
```

```

        endcase
    end
end

endmodule

// 2-to-1 MUX module
module mux2to1 (
    input wire sel,
    input wire i0,
    input wire i1,
    output reg f
);

    always @(*) begin
        case (sel)
            1'b0: f = i0;
            1'b1: f = i1;
        endcase
    end

endmodule

module Lab20301269 (
// Top module for the circuit in Figure 1
    input wire Enable,
    input wire Clk,
    input wire Reset,
    input wire mode_sel,
    output wire Q0,
    output wire Q0_bar,
    output wire Q1,
    output wire Q1_bar,
    output wire Q2,
    output wire Q2_bar,
    output wire Q3,
    output wire Q3_bar
);

    wire [3:0] sel_signals;
    wire [3:0] i0_signals;
    wire [3:0] i1_signals;
    wire [3:0] f_signals;
    wire [3:0] AND2_outputs;

```

```

// Generate select signals for the multiplexers
assign sel_signals[0] = mode_sel;
assign sel_signals[1] = mode_sel;
assign sel_signals[2] = mode_sel;
assign sel_signals[3] = mode_sel;

// Generate input signals for the multiplexers
assign i0_signals[0] = 1'b0;
assign i0_signals[1] = 1'b0;
assign i0_signals[2] = 1'b0;
assign i0_signals[3] = 1'b0;

assign i1_signals[0] = Q0;
assign i1_signals[1] = Q1;
assign i1_signals[2] = Q2;
assign i1_signals[3] = Q3;

// Instantiate multiplexers
mux2to1 mux_inst0 (.sel(sel_signals[0]),.i0(i0_signals[0]),.i1(i1_signals[0]),.f(f_signals[0]));
mux2to1 mux_inst1 (.sel(sel_signals[1]),.i0(i0_signals[1]),.i1(i1_signals[1]),.f(f_signals[1]));
mux2to1 mux_inst2 (.sel(sel_signals[2]),.i0(i0_signals[2]),.i1(i1_signals[2]),.f(f_signals[2]));
mux2to1 mux_inst3 (.sel(sel_signals[3]),.i0(i0_signals[3]),.i1(i1_signals[3]),.f(f_signals[3]));


// Instantiate AND2 gates
assign AND2_outputs[0] = Enable & f_signals[0];
assign AND2_outputs[1] = Enable & f_signals[1];
assign AND2_outputs[2] = Enable & f_signals[2];
assign AND2_outputs[3] = Enable & f_signals[3];
// Instantiate T Flip-Flops
T_FF TFF_inst0 (.clk(Clk),.reset(Reset),.T(AND2_outputs[0]),.Q(Q0),.Q_bar(Q0_bar));
T_FF TFF_inst1 (.clk(Clk),.reset(Reset),.T(AND2_outputs[1]),.Q(Q1),.Q_bar(Q1_bar));
T_FF TFF_inst2 (.clk(Clk),.reset(Reset),.T(AND2_outputs[2]),.Q(Q2),.Q_bar(Q2_bar));
T_FF TFF_inst3 (.clk(Clk),.reset(Reset),.T(AND2_outputs[3]),.Q(Q3),.Q_bar(Q3_bar));

endmodule


```

#####

RTL:

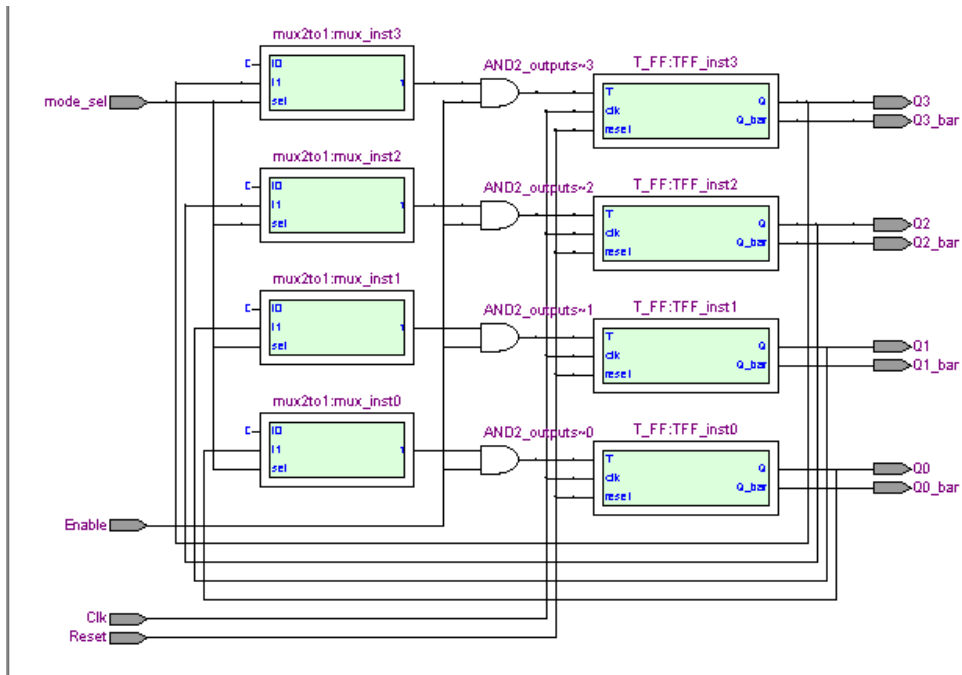

#####  
SIMULATION:

 

TRUTH TABLE:

Master Time Bar: 15.725 ns			Pointer:
	Name	Value at 15.73 ns	
0	Clk	A 0	
1	...able	A 1	
2	Q0	A 0	
3	..._bar	A 1	
4	Q1	A 0	
5	..._bar	A 1	
6	Q2	A 0	
7	..._bar	A 1	
8	Q3	A 0	
9	..._bar	A 1	
10	Reset	A 0	
11	..._sel	A 1	

	Clock	Reset	Select	Q0	Q1	Q2	Q3
0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0

0	0	0	0	1	0	0
---	---	---	---	---	---	---

1	0	0	1	1	0	0
---	---	---	---	---	---	---

0	0	0	0	0	1	0
---	---	---	---	---	---	---

1	0	0	1	0	1	0
---	---	---	---	---	---	---

0	0	0	0	1	1	0
---	---	---	---	---	---	---

1	0	0	1	1	1	0
---	---	---	---	---	---	---

0	0	0	0	0	0	1
---	---	---	---	---	---	---

1	0	0	1	0	0	1
---	---	---	---	---	---	---

0	1	0	0	0	0	0
						0
1	1	0	0	0	0	

#####

The Lab20301269 module has the following input-output pins:

- Enable: Enables or disables the T Flip-Flops
- Clk: Clock signal for the T Flip-Flops
- Reset: Reset signal for the T Flip-Flops
- mode\_sel: Selects the input to the multiplexers
- Q0, Q0\_bar, Q1, Q1\_bar, Q2, Q2\_bar, Q3, Q3\_bar: Outputs of the T Flip-Flops

The overall functionality of the Lab20301269 module is as follows:

- The multiplexers select the input to the T Flip-Flops based on the mode\_sel signal.
- The T Flip-Flops toggle their outputs based on the input from the multiplexers and the clock signal.
- The Enable signal enables or disables the T Flip-Flops.
- The Reset signal resets the T Flip-Flops to their initial state.
-



